

EEC 180 Lab 3

Bradley Manzo

916953788

Objective and Introduction:

The objective of this lab is to implement the full adder module from *Lab 2* and compare it with a golden reference program using a specialized testbench program.

Results:

Part II. Three 3-bit adder modules:

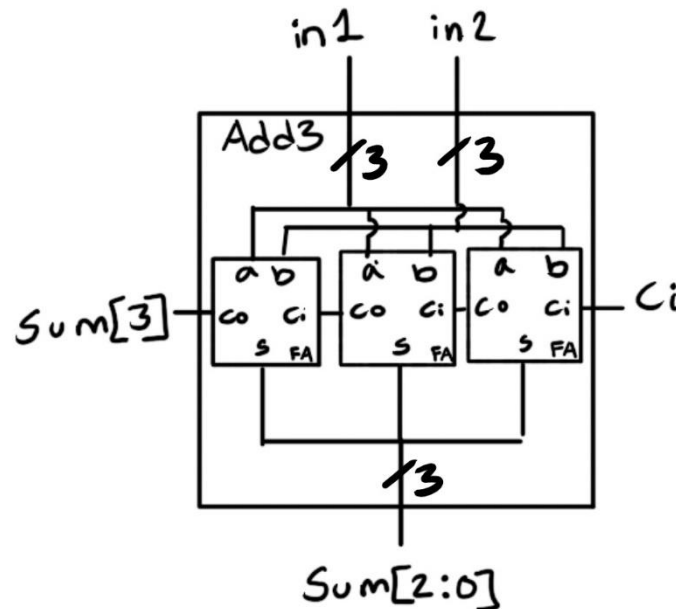


Figure 1: Add3 Circuit Diagram

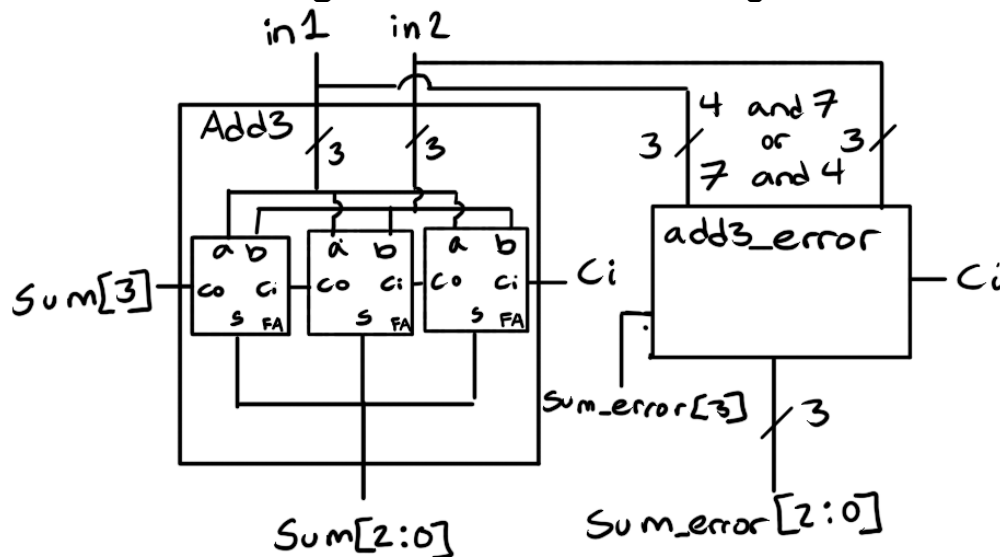


Figure 2: Add3_error Circuit Diagram

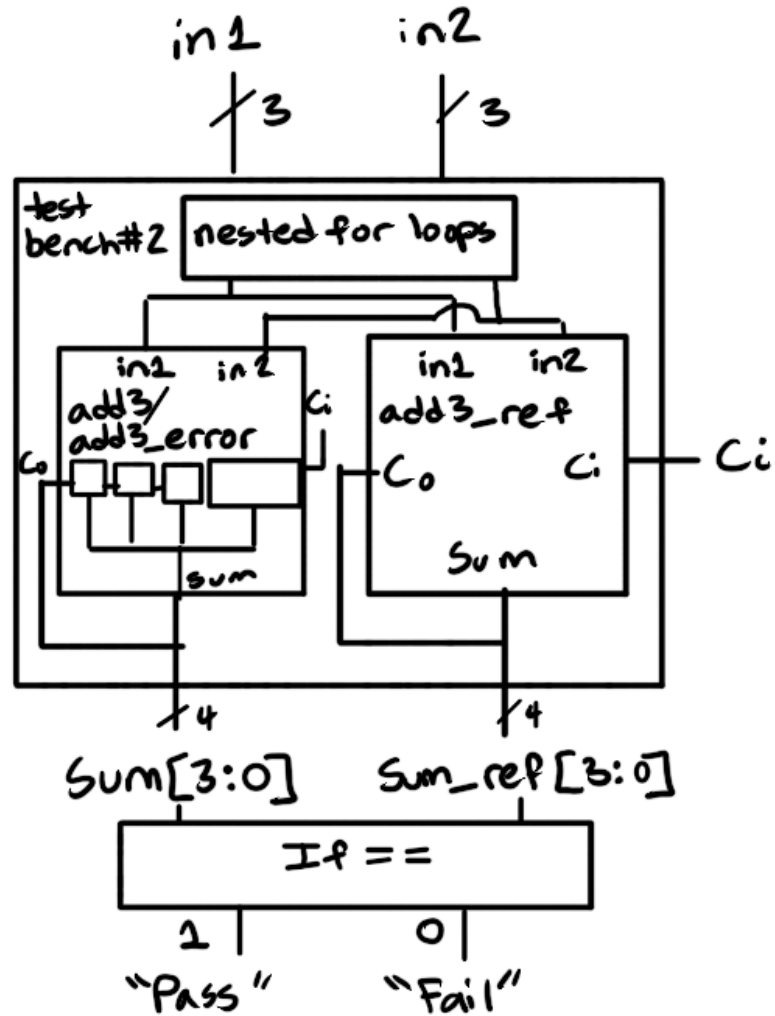


Figure 3: Testbench #2 Circuit Diagram

Part III. Testbench #1:

```

VSIM 8> run -all
# in1 = 0, in2 = 0, sum = 0
# in1 = 0, in2 = 1, sum = 1
# in1 = 1, in2 = 0, sum = 1
# in1 = 5, in2 = 5, sum = 10
# in1 = 7, in2 = 0, sum = 7
# in1 = 0, in2 = 7, sum = 7
# in1 = 7, in2 = 7, sum = 14
# in1 = 6, in2 = 2, sum = 8
# in1 = 3, in2 = 4, sum = 7
# in1 = 3, in2 = 1, sum = 4
# in1 = 7, in2 = 2, sum = 9
# in1 = 3, in2 = 3, sum = 6
# in1 = 3, in2 = 6, sum = 9
# in1 = 7, in2 = 2, sum = 9
# in1 = 3, in2 = 3, sum = 6

```

Figure 4: Text Printout from Part III A

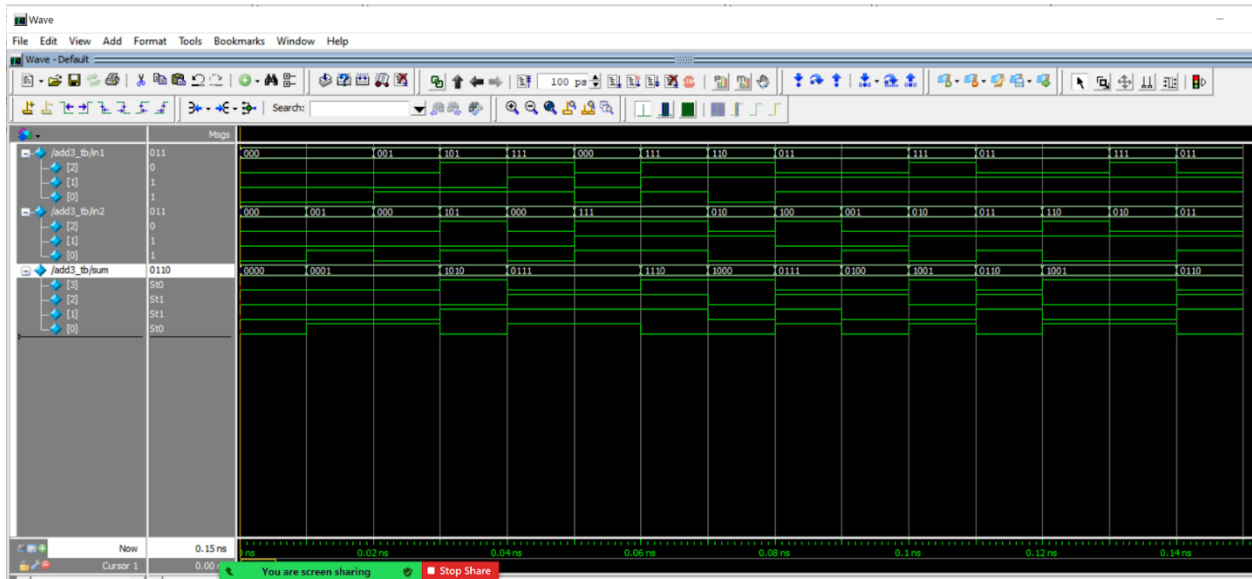


Figure 5: Waveform Printout from Part III B

Part IV. Testbench #2:

[illegible]

Figure 6: Text Printout from Part IV A

[illegible]

Figure 7: Text Printout from Part IV B

Conclusion:

After completing lab 3, I feel I have gained a greater understanding of a golden reference's importance with testing a circuit, and I feel I am now prepared to design more competent testbenches and golden references for future labs.